

Cool-Emerald

Our thoughts and memories...

Sasana Year 2566 , Myanmar Year 1384 , Tabodwe waxing 5 , Wednesday .

[Home](#)[Contact Us](#)[Profile](#)[About](#)

Thursday, May 5, 2016

DRV2700 Piezo Driver

DRV2700 is a single chip Piezo driver which is 4 mm x 4 mm x 0.9 mm in size. It can be used in 100 V boost or 1 kV flyback configuration. Supply voltage is 3 V - 5.5 V. In this article, evaluation of **DRV2700EVM** module is discussed.

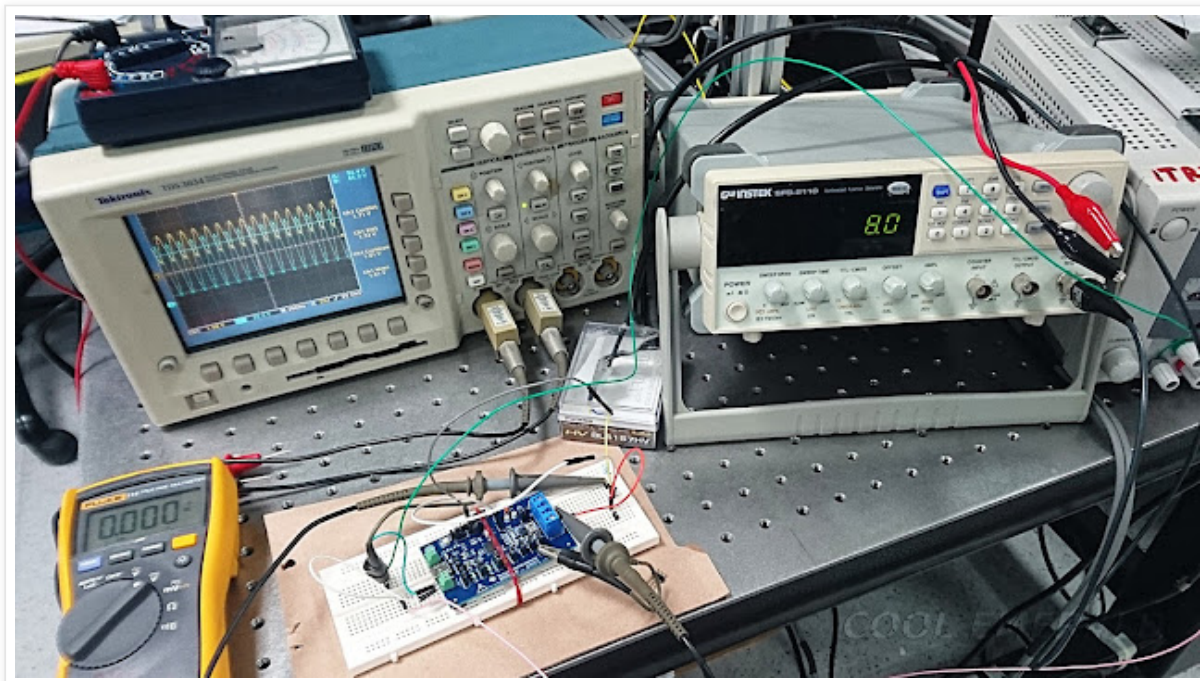


Figure. Testing DRV2700.

The following figure illustrate boost + amplifier configuration of DRV2700.

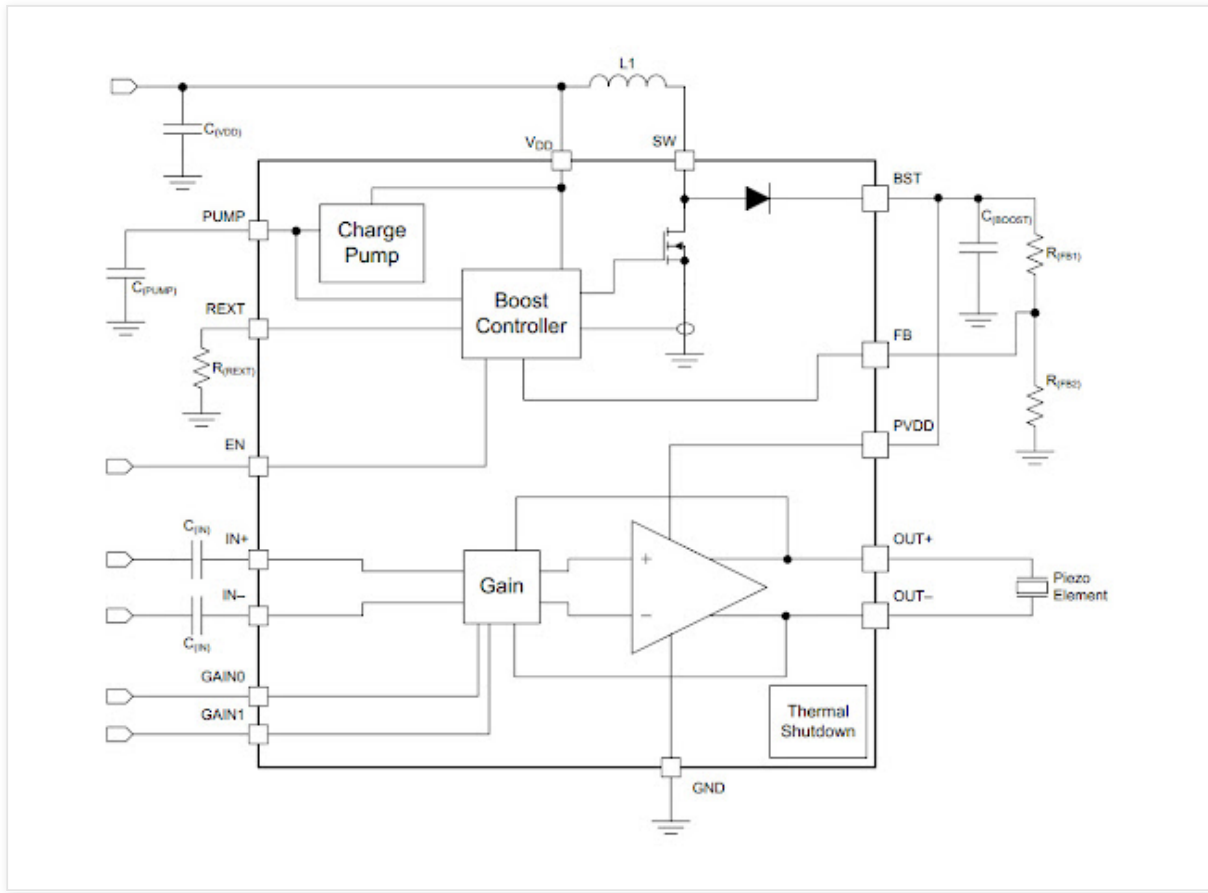


Figure. DRV2700 boost + amplifier configuration.

Where BST is boost output voltage. BST is used as supply voltage (PVDD) for the amplifier. EN is chip enable. FB is boost feedback used together with R_{FB1} and R_{FB2} to produce required boost voltage. $V_{FB} = 1.3 \text{ V}$ and, the relation between R_{FB1} , R_{FB2} , and V_{BST} in boost + amplifier configuration is as follow.

$$V_{BST} = V_{FB} \left(1 + \frac{R_{FB1}}{R_{FB2}} \right)$$

For example, if we want V_{BST} of 105 V, we can use $R_{FB1} = 806 \text{ k}\Omega$ and $R_{FB2} = 10.1 \text{ k}\Omega$. When $R_{FB1} = 806 \text{ k}\Omega$ and $R_{FB2} = 16.45 \text{ k}\Omega$, V_{BST} will be 65 V. Jumper settings and V_{BST} table for Evaluation module DRV2700EVM is shown below.

BST	R _{EQ}	JP2	JP3	JP4
23 V	50 kΩ	Open	Open	Open
37 V	30.8 kΩ	Open	Open	Closed
45 V	25 kΩ	Open	Closed	Open
58 V	19.0 kΩ	Open	Closed	Closed
70 V	15.7 kΩ	Closed	Open	Open
83 V	13.2 kΩ	Closed	Open	Closed
91 V	12 kΩ	Closed	Closed	Open
105 V	10.4 kΩ	Closed	Closed	Closed

Figure. BST Setting Based on the Jumper Configuration.

GAIN0 and GAIN1 pins define the gain of amplifier which is $(\frac{OUT^+ - OUT^-}{IN^+ - IN^-})$.

Table. Amplifier gain

GAIN[1:0]	G _{dB}	G _{AMP}
00	28.8	27.54
01	34.8	54.95
10	38.4	83.18
11	40.7	108.4

The performance of DRV2700 largely depends on the choice of inductor also. The recommended values for the inductor is between 3.3 μH and 22 μH. In general, the smaller the inductance, the higher the saturation current limit. When a large inductance value is used, DRV2700 will automatically switch to lower switching frequency which gives smaller switching losses. On the other hand, it will has higher parasitic inductor losses. Typically, smaller inductance values are used to obtain higher current limit. In this evaluation module, 4.7 μH, 2.7 A inductor is used.

R_{EXT} is used to limit boost current by connecting a resistor to ground. The value of resistor should be between 6 kΩ and 35 kΩ. The relationship between Current limit (I_{LIM}) and resistor (R_{EXT}) is shown below, where K=10500, V_{REF}=1.35 V, and R_{INT}=60 Ω.

$$R_{EXT} = K \cdot \frac{V_{REF}}{I_{LIM}} - R_{INT}$$

For example, when R_{EXT}=6.04 kΩ, I_{LIM} will be 2.32 A. To obtain I_{LIM} = 1 A, the value of R_{EXT} should be 14 kΩ.

The minimum value of boost capacitor should be 50 nF. X7R type 100 nF capacitor is recommended. It is found that the lower the boost voltage, the better the efficiency. The efficiency at 80 V is around 50 % as shown in the following charts.

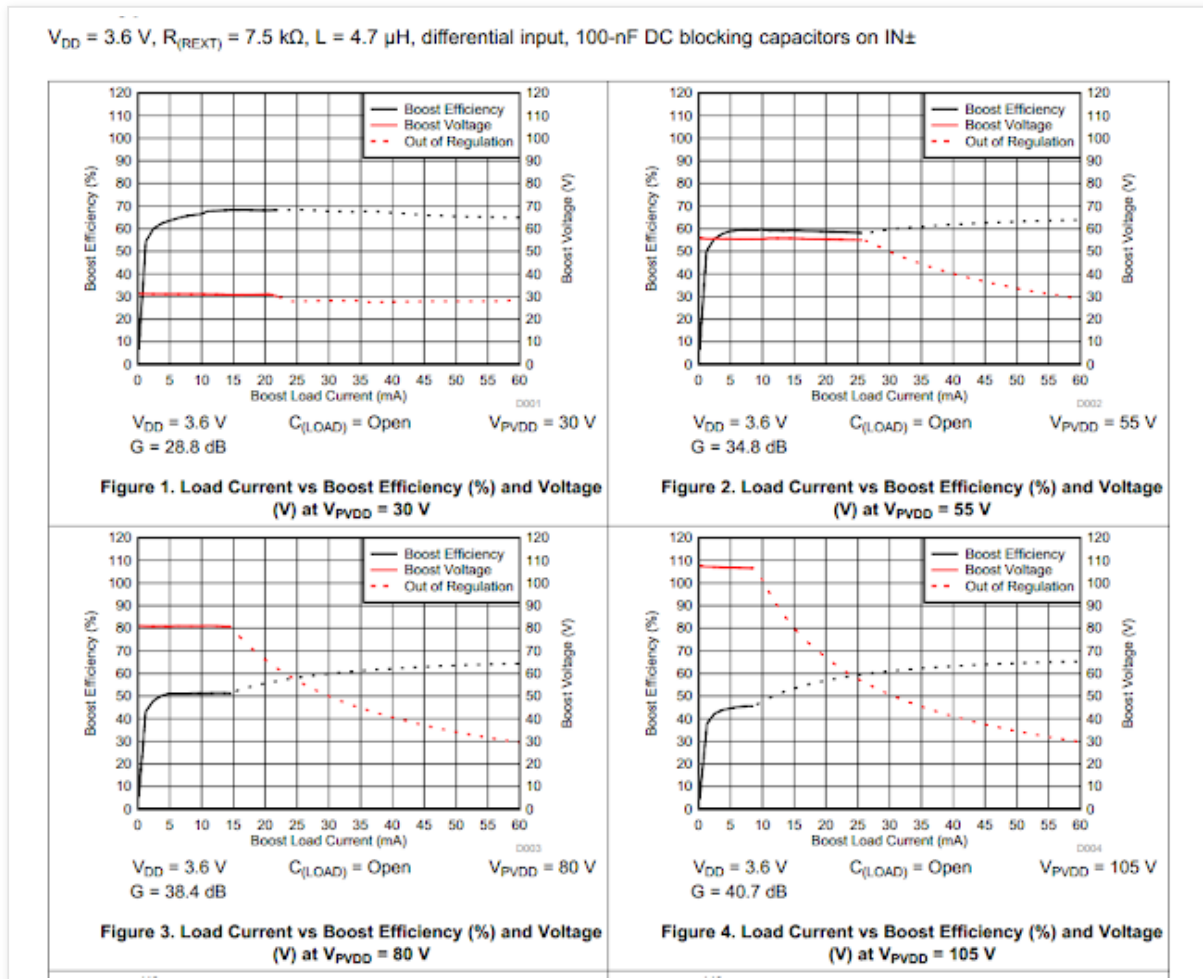


Figure. Typical characteristics.

A system example which uses DC coupled input is shown below.

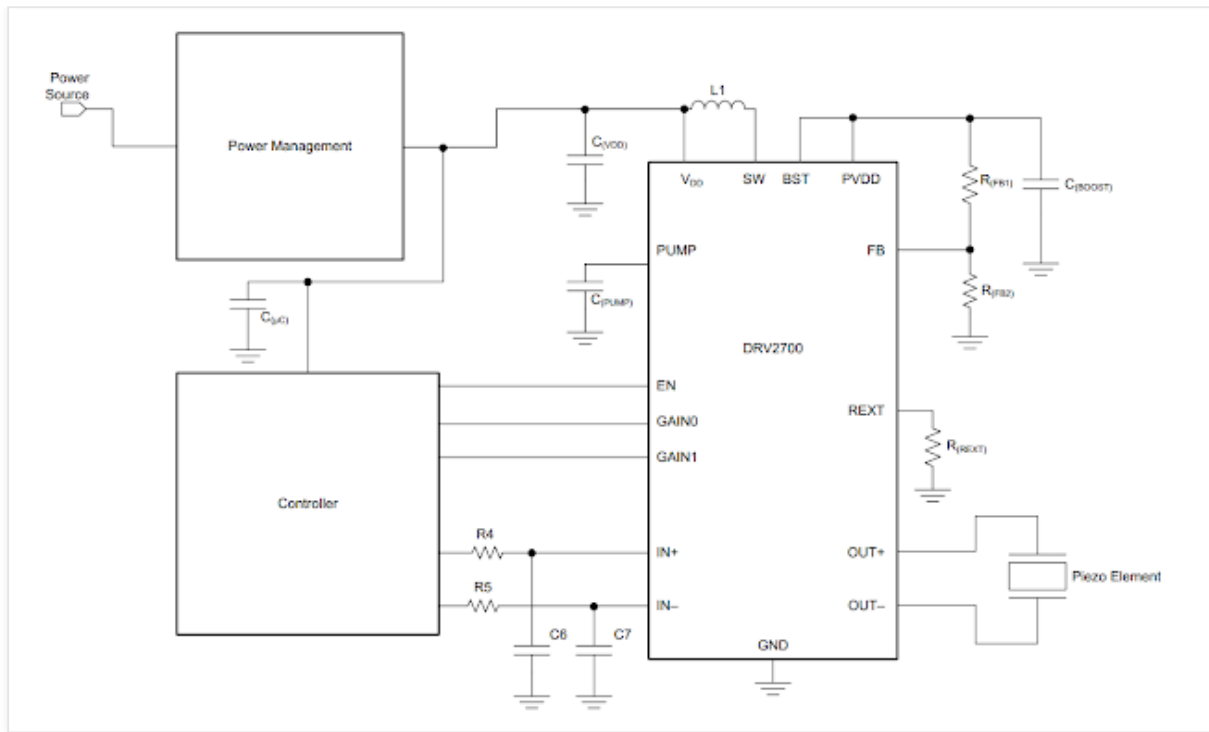


Figure. DC coupled DAC input configuration.

A piezo element can be modeled as a capacitor. Then, the peak value for its load current - I_{peak} can be calculated as follow.

$$I_p = 2 \cdot \pi \cdot f \cdot C \cdot V_p$$

If you want the value of peak supply current for DRV2700, I_{DD} , the voltage ratio, and efficiency - μ can be used to calculate as follow.

$$I_{DD} = 2 \cdot \pi \cdot f \cdot C \cdot V_p \cdot \frac{V_{BST}}{V_{DD} \cdot \mu}$$

For example, [Stack Multilayer Piezo Actuator, PICMA P-885.91](#) (Physik Instrumente, Karlsruhe, Germany) has capacitance 3.1 μF and travel range 32 μm . For $V_p = 50 \text{ V}$ and frequency 10 Hz, I_{peak} is 9.7 mA. Using $V_{BST} = 105 \text{ V}$, $V_{DD} = 3.3 \text{ V}$, and efficiency $\mu = 45\%$, peak I_{DD} is obtained as 689 mA.

As an another example, [Noliac plate stack actuator NAC2003-H50-A01](#) has capacitance 24620 nF and travel range 72 μm . For $V_p = 30 \text{ V}$ and frequency 10 Hz, I_{peak} is 46.4 mA. Using $V_{BST} = 65 \text{ V}$, $V_{DD} = 3.3 \text{ V}$, and efficiency $\mu = 55\%$, peak I_{DD} will be 1.66 A.

DRV2700 is compared against [DRV8662](#) which is used in [PDU100D](#). For Piezo actuator with large capacitive load, DRV2700 is said to be more suitable.

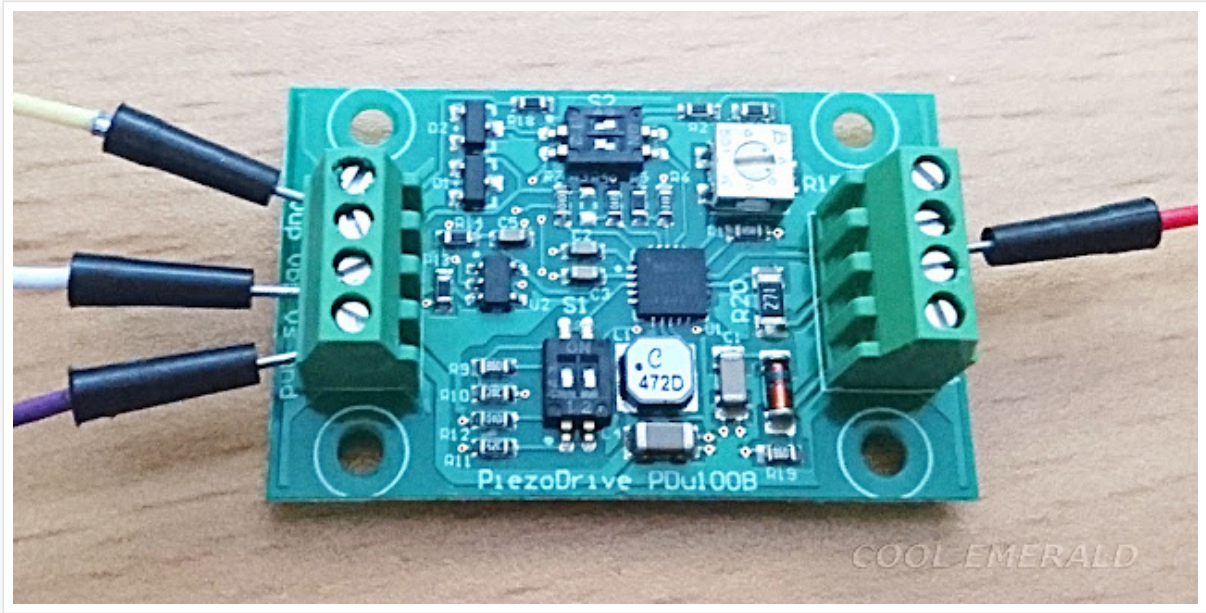


Figure. pDu100B

To reduce noise at output voltage, output resistor R_o is normally used to connect piezo element in series. Bandwidth is same as that of first order RC low pass filter.

$$f_c = \frac{1}{2.\pi. R_o. C}$$

The result of comparison between these two piezo drivers is shown below.

Table. Driving NAC2003-H50-A01, 25 μ F with 60V peak to peak sinusoidal @ V_{BST} = 60 V, V_{DD} = 5 V, R_o = 1 k Ω


Driver	DC	1 Hz	10 Hz
DRV2700	13.5 mA	10 ~ 110 mA	170 ~ 250 mA
pDu100B	33 mA	30 ~ 130 mA	200 ~ 300 mA

Table. Driving PICMA P-885.91, 3 μ F with 60V peak to peak sinusoidal @ V_{BST} = 100 V, V_{DD} = 5 V, R_o = 1 k Ω

Driver	DC	1 Hz	10 Hz
DRV2700	34 mA	32 ~ 57 mA	120 ~ 167 mA
pDu100B	73 mA	80 ~ 125 mA	160 ~ 220 mA

I have designed a 3 channel piezo driver which is shown in the following figure. It uses three

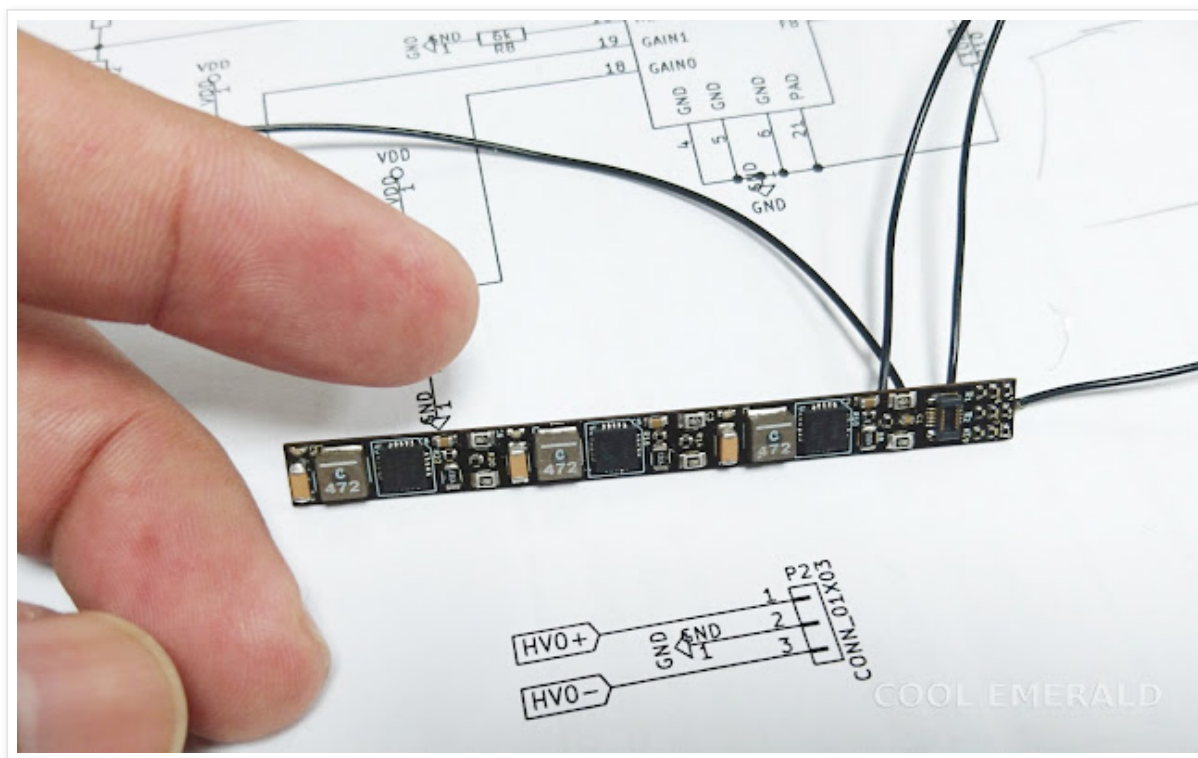DRV2700. It is 4 layered PCB with only 6 mm x 69 mm in size.



Posted by Yan Naing Aye at [Thursday, May 05, 2016](#)



Labels: [Amplifier](#), [Driver](#), [DRV2700](#), [Electronics](#), [Piezoelectric](#)

No comments:

Post a Comment

Comments are moderated and don't be surprised if your comment does not appear promptly.



Enter Comment

[Newer Post](#)

[Home](#)

[Older Post](#)

Subscribe to: [Post Comments \(Atom\)](#)

Blog Archive

► [2022](#) (5)

► [2021](#) (5)

► [2020](#) (12)

- ▶ 2018 (12)
- ▶ 2017 (13)
- ▼ 2016 (10)
 - ▶ December (1)
 - ▶ August (1)
 - ▶ July (1)
 - ▼ May (2)
 - DS1307 Real-time Clock
 - DRV2700 Piezo Driver
 - ▶ April (3)
 - ▶ March (1)
 - ▶ January (1)
- ▶ 2015 (7)
- ▶ 2014 (6)
- ▶ 2013 (14)
- ▶ 2012 (4)
- ▶ 2011 (11)
- ▶ 2010 (10)
- ▶ 2009 (10)
- ▶ 2008 (11)

Labels

.NET 2.4 GHz 2005 6 DOF 6DoF 8051 A4988 Accelerometer
Actuator Adaptive Filter ADC ADS1115 Aircon AJAX Algorithm
Amplifier Arduino ARM Armbian Astrological AT89C51CC03
barcode BeagleBoard BeagleBone Bibliography Bluetooth BMFLC
Book Burmese byte stuffing C C++ Calendar CAN Capacitor
CC2530 CCTV Centroid of Myanmar Circuit Clock CMake
CMUcam5 Code Code::Blocks CodeLite Color Com Comm
Communication Compensation Computer Vision Control
CoreXY cpprestsdk CRC Cross-compiling Cross-platform CRP Crystal
Oscillator Current Transformer Curve Fitting D-H model DAC
Database Daughters Device Driver Diode Discrete Backlash
Operator DIY DLL DOF DrawBot Driver DRV2700 DRV8825
DRV8834 DS1307 Dynamic Link Library Electronics email
Embedded System Encoder Energy Ethernet face-detection
Family FAT32 Feed-forward firmware Flash Fourier FRDM-
K64F FRDM-K82F Free Software FreeTDS Freeware Fujitsu
Function generator Fusion g++ galaxy note 2 gcc gcode GIMP
Gnuplot grbl Gregorian Gyroscope Haar Cascades Hardware
HDR Health HFMD High pass filter Human Arm Hysteresis I2C IAR
IEEE 802.15.4 ILI9341 image Image processing IMU
Inertial Measurement Unit Inkscape Integration Interface internet
interrupt JavaScript JN5168 JSON JsonCpp Julian k-means K64
K82 KiCad Kids Kinematics L3G4200D LabVIEW Laser LaTeX
LCD Linux LM337 LM358N Low pass filter LPC54102 LPC824
LPCXpresso824-MAX LuaTeX Mathematics MatLab Matplotlib

MCP3008 MCU MCUXpresso Mechanical Mechatronics
Medical Mesh Bee Meter **Microcontroller** ModBus
Model Monitor Monte Carlo Integration Motor Driver MsSQL multidrop
multithreading Myanmar MySQL Network NotifyIcon NXP **Octave**
ODBC Odroid Op-amp op-amp oscillator Open source **opencv**
opencv-3.2.0 opencv3 OPI Orange Pi Parallel Port password
pca9535 PCB PCF8591 personal phone **Photography**
Piezoelectric PIR Sensor Pixy pkg-config Prandtl-Ishlinskii
Programming Qt Raspberry Pi RaspiCam RC real-
time Reference Regulator Relay repair REST robot **Robotics**
Rotation RS232 RS422 RS485 SB-900 SBC schroot SD Card
SDCC Sensor Serial **Serial Port** **Signal Processing** Simple
Smart Home Socket soft-timer SPI SQL Stages Stepper Motor
Surveillance SVG System TCP Template tesseract tesseract-ocr
TeXstudio Thesis TI Timer Tool Touch Transceiver Translation
Travel **UART** Ubuntu UDP USB v4l2 VB vector graphic Velvia
Virtual Com **Visual Basic** Visual Studio Visual Studio 2015 VNC
VS14 Web Windows **Wireless** Writing wxDev-C++ wxJSON
wxWidgets X DevAPI XeLaTeX XeTeX XY Plotter Zigbee zint

00053365

Powered by **Blogger**.